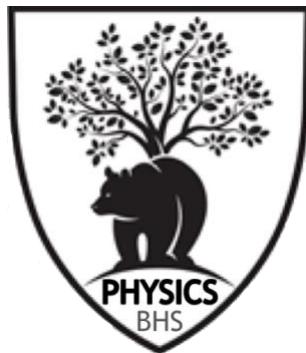


# Electricity Block 2

## Electronics

### Knowledge Organizer

Key: [PHY] = National 5 Physics (Electricity) - [PE] = National 5 Practical Electronics - [BOTH] = appears in both



#### TABLE OF CONTENTS

<b>Electricity Block 2</b> .....	1
<b>Electronics</b> .....	1
<b>Knowledge Organizer</b> .....	1
<b>Core electrical ideas (B2 focus)</b> .....	2
1) Key quantities and units.....	2
2) Essential equations (B2) .....	2
3) Series and parallel recap (from Block 1 - Electricity B1) .....	2
<b>Components you must recognise (B2 set)</b> .....	2
4) Power connections and switches .....	2
5) Resistors, meters and output devices .....	3
6) Diodes, LEDs, capacitors and sensors.....	3
<b>Potential dividers, LEDs and control circuits</b> .....	4
7) Potential divider (core B2 idea) .....	4
8) Quick rules (IF...THEN...) .....	4
9) LED protective resistor (current limiting).....	4
10) Control circuits (using LDR/thermistor + divider + switch stage) .....	5
<b>Switching, simulation, testing and soldering</b> .....	6
12) Transistors and MOSFETs used as switches .....	6
13) Yenka (simulation) – quick purpose.....	6
14) Testing mindset (electronics) .....	6
15) Common mistakes (fault-finder box).....	7
16) Soldering and tools (definitions) .....	7

## CORE ELECTRICAL IDEAS (B2 FOCUS)

### 1) KEY QUANTITIES AND UNITS

Idea	Definition	Unit	Course link
Electric current (I)	The <b>rate of flow of electric charge</b> in a circuit.	ampere (A)	[BOTH]
Electric charge (Q)	The amount of electric charge transferred.	coulomb (C)	[BOTH]
Potential difference / voltage (V)	The <b>energy transferred per coulomb of charge</b> between two points in a circuit.	volt (V)	[BOTH]
Resistance (R)	A measure of how much a component <b>opposes the flow of current</b> .	ohm ( $\Omega$ )	[BOTH]

Note: Power and energy are covered in **Block 3**, so they are not included here.

### 2) ESSENTIAL EQUATIONS (B2)

Equation (SQA notation)	What it's for	Notes	Course link
$Q = I t$	Charge transferred in time $t$	$t$ in seconds (s)	[BOTH]
$V = I R$	Ohm's law calculations	Valid for <b>ohmic</b> components (straight-line V-I graph)	[BOTH]
$V_2 = \frac{R_2}{R_1 + R_2} V_s$	Potential divider output voltage across $R_2$	$R_1$ and $R_2$ in series; $V_2$ is across $R_2$	[BOTH]
$\frac{V_1}{V_2} = \frac{R_1}{R_2}$	Divider relationship (ratio form)	Useful for comparing changes	[BOTH]

### 3) SERIES AND PARALLEL RECAP (FROM BLOCK 1 - ELECTRICITY B1)

Rule (B1 recap)	Summary	Course link
Series	Current same everywhere; voltages add.	[BOTH]
Parallel	Voltage same across branches; current splits.	[BOTH]

### COMPONENTS YOU MUST RECOGNISE (B2 SET)

### 4) POWER CONNECTIONS AND SWITCHES

Component	Function (what it does)	Typical use / example	Symbol/diagram box	Course link
Voltage rails ( $V+$ and $0V/-$ )	The <b>supply connections</b> used to power a circuit (often shown as rails/lines on diagrams or breadboards).	Powering a breadboard or stripboard circuit	+5V —	[BOTH] (used heavily in [PE])
Switch (SPST)	Single pole single throw: ON/OFF switch that opens or closes one path.	Simple on/off control		[BOTH]


Switch (SPDT)	Single pole double throw: connects one input to <b>one of two outputs</b> .	Selecting between two paths (eg two control modes)		[BOTH] (used heavily in [PE])
---------------	---	--	--	----------------------------------

## 5) RESISTORS, METERS AND OUTPUT DEVICES

Component	Function (what it does)	Typical use / example	Symbol box	Course link
Resistor (fixed)	Limits current / creates a voltage drop.	Current limiting, potential dividers		[BOTH]
Variable resistor	Adjustable resistance.	Sensitivity/threshold control in a divider		[BOTH] (applications deeper in [PE])
Ammeter	Measures current (connected in series).	Measuring circuit current		[BOTH]
Voltmeter	Measures potential difference (connected in parallel).	Measuring voltage across a component		[BOTH]
Lamp	Converts electrical energy to light (and heat).	Indicator / lighting		[BOTH]
Motor	Converts electrical energy to kinetic energy.	Fans, mechanisms		[BOTH]
Loudspeaker / buzzer	Converts electrical energy to sound.	Sound output / alarms		[BOTH] (buzzer often used in [PE])


## 6) DIODES, LEDs, CAPACITORS AND SENSORS

Component	Definition / key idea	What to remember	Symbol box	Course link
Diode	Allows current to flow in <b>one direction only</b> .	Forward bias conducts; reverse bias blocks.		[BOTH]
LED (light emitting diode)	A diode that emits light when current flows forward.	Needs a <b>protective resistor</b> to limit current.		[BOTH]
Capacitor	Stores electric charge and energy.	Used for <b>timing and smoothing</b> (applications emphasised in [PE]).		[BOTH]

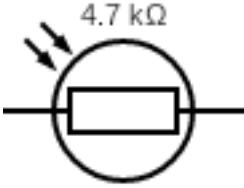LDR (light dependent resistor)	Resistance depends on light level.	More light → lower resistance (typical).		[BOTH]
Thermistor (NTC)	Resistance depends on temperature.	Higher temperature → lower resistance (typical NTC).		[BOTH]

## POTENTIAL DIVIDERS, LEDS AND CONTROL CIRCUITS

### 7) POTENTIAL DIVIDER (CORE B2 IDEA)

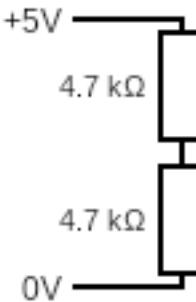Topic	Student-ready notes	Diagram box	Course link
What is a potential divider?	Two (or more) resistors in series used to create an output voltage that is a fraction of the supply voltage.		
Naming	$V_s$ = supply voltage. $R_1$ and $R_2$ are the series resistors. $V_2$ is the output voltage across $R_2$ .		
Why do we use it?	To make a variable voltage signal. Using an LDR/thermistor/variable resistor makes the output voltage change with light/temperature/setting.		[BOTH]
Divider equation	$V_2 = \frac{R_2}{R_1 + R_2} V_s$		
Key understanding	The resistor with the bigger share of total resistance gets the bigger share of the supply voltage.		

### 8) QUICK RULES (IF...THEN...)

Quick rule	Meaning in words	Course link
If $R_2$ increases → $V_2$ increases	A bigger $R_2$ gives a bigger fraction of $V_s$ across $R_2$ .	[BOTH]
If $R_1$ increases → $V_2$ decreases	More of $V_s$ is “used up” across $R_1$ , leaving less across $R_2$ .	[BOTH]
LDR: light level increases → resistance decreases	Bright light makes an LDR’s resistance drop.	[BOTH]
NTC thermistor: temperature increases → resistance decreases	Hotter thermistor → lower resistance (NTC).	[BOTH]

### 9) LED PROTECTIVE RESISTOR (CURRENT LIMITING)




Topic	Student-ready notes	Course link
Why an LED needs a resistor	LEDs don’t limit current well; without a resistor the current can be too large and damage the LED.	[BOTH]
Resistor calculation	$R = (V_s - V_{LED}) / I_{LED}$	

## 10) CONTROL CIRCUITS (USING LDR/THERMISTOR + DIVIDER + SWITCH STAGE)

Circuit type	What it means	What changes the output	Diagram box	Course link
High light control	Output turns <b>ON</b> at <b>high light level</b> .	LDR resistance changes → divider output voltage changes → switch stage changes output.		[PE]
Low light control	Output turns <b>ON</b> at <b>low light level</b> .	LDR resistance changes → divider output voltage changes → switch stage changes output.		[PE]
High temperature control	Output turns <b>ON</b> at <b>high temperature</b> .	Thermistor resistance changes → divider output voltage changes → switch stage changes output.		[PE]
Low temperature control	Output turns <b>ON</b> at <b>low temperature</b> .	Thermistor resistance changes → divider output voltage changes → switch stage changes output.		[PE]

## SWITCHING, SIMULATION, TESTING AND SOLDERING

### 12) TRANSISTORS AND MOSFETS USED AS SWITCHES

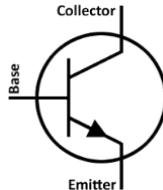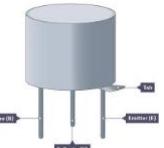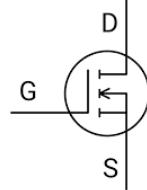Device	Definition	What to remember	Symbol box	Component	Course link
NPN transistor (BJT)	Semiconductor device that can act as an electronic switch.	A small <b>base current</b> controls a larger <b>collector current</b> . A silicon transistor typically begins to switch on when $V_{BE} \approx 0.7 \text{ V}$ (approx).			[BOTH] (skills/building focus is [PE])
n-channel enhancement MOSFET	Switch device controlled by <b>gate voltage</b> .	Very small gate current; turns on when the <b>gate voltage</b> is high enough (threshold behaviour).			[BOTH] (skills/building focus is [PE])

### 13) YENKA (SIMULATION) – QUICK PURPOSE

Yenka	<p><b>Test circuits safely</b> before building</p> <p><b>Measure voltages/currents</b> without risk</p> <p><b>Compare</b> results to your calculations</p> <p><b>Practice fault finding</b> using “normal” readings as a reference</p>	<b>Course link:</b> [PE]
-------	--	--------------------------

### 14) TESTING MINDSET (ELECTRONICS)

Test stage	What it means	Examples	Course link
Pre-power-up checks	Checks done <b>before switching on</b> to avoid damage.	Correct component values; correct orientation (diode/LED/capacitor/transistor); no loose wires; no short circuits; correct power connections; tidy wiring.	[PE]
Functionality tests	Tests done <b>after switching on</b> to confirm the circuit works.	Measure supply voltage; measure key node voltages; confirm output turns on/off in the correct conditions; compare to simulation; check current isn't excessive.	[PE]

## 15) COMMON MISTAKES (FAULT-FINDER BOX)

Common mistake	What you usually see	Quick fix	Course link
LED reversed	LED never lights	Flip LED orientation (check diode direction)	[PE]
No protective resistor	LED very bright then fails / gets hot	Add correct series resistor	[PE]
Measuring the wrong voltage	Numbers don't match expectation	Measure <b>V2</b> across <b>R2</b> (parallel connection)	[BOTH]
Wrong rail / no 0 V reference	Circuit behaves unpredictably / no output	Check V+ and 0 V rails are correct and continuous	[PE]
Short circuit / solder bridge	Supply drops / components heat / output stuck	Inspect, rework solder, remove bridge with solder sucker	[PE]
Transistor/MOSFET pins mixed up	Switch stage doesn't work	Re-check pinout (E/B/C or G/D/S) before powering	[PE]

## 16) SOLDERING AND TOOLS (DEFINITIONS)

Item	Definition / purpose	Safety / good practice	Course link
Track cutter	Tool used on stripboard to <b>break a copper track</b> so parts of the circuit are electrically separated.	Double-check the correct hole/track before cutting.	[PE]
Heat sink	A clip/metal part used to <b>carry heat away</b> from a component while soldering.	Protects heat-sensitive components; don't overheat parts.	[PE]
Solder sucker	Tool used to <b>remove molten solder</b> to fix mistakes or clear holes.	Use carefully; keep iron tip clean and tinned.	[PE]
Good solder joint	A clean, shiny joint that securely connects component and pad/track.	Right amount of solder; heat the joint not the solder; keep parts still while cooling.	[PE]