



National  
Qualifications

---

**X860/75/01**

**Practical Electronics**

## **Marking Instructions**

---

Please note that these marking instructions have not been standardised based on candidate responses. You may therefore need to agree within your centre how to consistently mark an item if a candidate response is not covered by the marking instructions.

## General marking principles for National 5 Practical Electronics

*This information is provided to help you understand the general principles you must apply when marking candidate responses to questions in this paper. These principles must be read in conjunction with the detailed marking instructions, which identify the key features required in candidate responses.*

- (a) Marks for each candidate response must **always** be assigned in line with these general marking principles and the detailed marking instructions (MIs) for this assessment.
- (b) Marking should always be positive. This means that, for each candidate response, marks are accumulated for the demonstration of relevant skills, knowledge and understanding: they are not deducted from a maximum on the basis of errors or omissions.
- (c) If a specific candidate response does not seem to be covered by either the principles or detailed marking instructions, and you are uncertain how to assess it, you must seek guidance from your team leader.

When marking National 5 Practical Electronics, there are some common issues which arise when considering candidates' answers.

There is often a range of acceptable answers which would sensibly answer a particular question. However, it is often difficult to anticipate all correct or partially correct responses to questions.

The answers given in the MIs represent ideal answers.

Additional acceptable answers are also given in the MIs to offer guidance to assist interpreting candidates' answers.

Also, advice on answers which are NOT acceptable or only attract partial marks may also be given in the MIs for some questions.

Markers are reminded that marks for each candidate response must always be assigned in accordance with the general marking principles and the specific marking instructions for the relevant question

- (d) There are **no half marks** awarded.
- (e) **In calculations**, marks should be awarded for non-standard symbols where the symbols are defined and the relationship is correct, or where the substitution shows that the relationship used is correct. This must be clear and unambiguous.
- (f) Unless a numerical question specifically requires evidence of working to be shown, full marks should be awarded for a correct final answer (including units if required) on its own.
- (g) Marks are provided for knowledge of relevant formulae alone. When a candidate writes down several formulae and does not select the correct one to continue with, for example by substituting values, no mark can be awarded.
- (h) Where a wrong answer to part of a question is carried forward and the wrong answer is then used correctly in the following part, the candidate should be given credit for the subsequent part or 'follow on'.
- (i) Rounding to an expected number of significant figures, the mark can be awarded for answers which have up to two figures more or one figure less than the number in the data with the fewest significant figures. (Note: the use of a recurrence dot, eg  $\dot{3}$ , would imply an infinite number of significant figures and would therefore not be acceptable.)
- (j) Where a question asks for or requires a specific number of reasons, examples, points, etc and the candidate provides more than the required number of responses then each incorrect response negates a correct response.

- (k) Marks are awarded only for a valid response to the question asked. For example, in response to questions that ask candidates to:
- **identify, name, give, or state**, they need only name or present in brief form;
  - **draw**, they must provide or complete a drawing, eg a circuit diagram, layout diagram or logic diagram;
  - **complete**, they must complete the response, eg completing a truth table, layout diagram, checklist, etc;
  - **describe**, they must provide a statement or structure of characteristics and/or features;
  - **explain**, they must relate cause and effect and/or make relationships between things clear;
  - **determine or calculate**, they must determine a number from given facts, figures or information;
  - **estimate**, they must determine an approximate value for something;
  - **justify**, they must give reasons to support their suggestions or conclusions, eg this might be by identifying an appropriate relationship and the effect of changing variables;
  - **show that**, they must use electronics (and mathematics) to prove something, eg a given value – *all steps, including the stated answer, must be shown*;
  - **predict**, they must suggest what may happen based on available information;
  - **suggest**, they must apply their knowledge and understanding of electronics to a new situation. A number of responses are acceptable: marks will be awarded for any suggestions that are supported by knowledge and understanding of electronics.

### Common issues with candidate responses:

#### Spelling

The incorrect spelling of technical terms should be ignored and candidates should be awarded the relevant mark. If answers can be interpreted and understood without any doubt as to the meaning, then the answer should be marked according to the MIs.

However, care should be taken to ensure that the incorrect spelling does not make the response ambiguous, leading to possible 'wrong electronics'. For example 'use a smaller resistor' instead of 'use a smaller resistance' is ambiguous, since a smaller resistor may not have a smaller resistance.

If the spelling (or handwriting) in an answer makes it difficult for you to interpret a candidate's intention, then do not award the mark.

#### Units

Use of R notation is acceptable eg 270R, 4k7, 6M8, etc.

For **numerical** and **non-numerical** answers which require a unit to be **stated** in an answer, the incorrect spelling of the unit is not usually penalised (if the unit can be clearly identified).

eg 'State the unit of capacitance.' Answer: 'farad'. The answer: 'farrads' would be acceptable.

Also for **numerical** and **non-numerical** answers, do not penalise upper/lower casing when the abbreviated version is given eg v, f, hZ.

Ohms ( $\Omega$ ) is an exception,  $\omega$  would not be an acceptable abbreviation.

However, for **numerical answers**, care must be taken to ensure the unit has the correct prefix, eg for an answer  $t = 0.005$  seconds,  $t = 5$  ms is acceptable but NOT  $t = 5$  Ms.


Some common units often attract wrong abbreviations in answers to numerical questions. When the abbreviation can be confused with a different unit then this would attract a unit penalty, eg sec or secs as an abbreviation for seconds is NOT acceptable.

### Standard form:

Candidates may fail to express an answer in standard form correctly.

For an answer  $t = 400\,000\text{ s}$ , then  $t = 4 \times 10^5\text{ s}$  would be correct but  $t = 4^5\text{ s}$  would be treated as an arithmetic error and the final mark would not be awarded.

### Relationship (equation) selection:

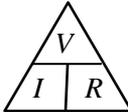No marks should be awarded if a 'magic triangle', eg , was the only statement in a candidate's response.

The correct relationship must be stated, eg  $V = IR$  or  $R = \frac{V}{I}$ , to gain (1) mark.

### Incorrect answer carried forward:

Where an incorrect answer to a part of a question is carried forward

- within that part of the question, eg (a)(i) and (a)(ii)
- to the next part of the question, eg (a) and (b)

this should incur no further penalty, provided that it is used correctly.

Where a question requires a data value and the candidate has selected the wrong value, then either the candidate's wrong value may be used OR the correct data value in the subsequent answer and the response could gain full marks if correctly completed.

### Example:

(a) State the tolerance in the resistance of a resistor with a gold tolerance band.

Candidate's answer: 2%. This answer would attract zero marks.

(b) Calculate the maximum and minimum possible resistances of the resistor.

Candidate may use either the value given in part (a) OR the correct value for the tolerance and could gain full marks if correctly completed.

The 'Additional guidance' column of the MIs would indicate the comment 'or consistent with part...' to indicate that an incorrect answer may be carried forward.

### Standard three marker:

The examples below set out how to apportion marks to answers requiring calculations. These are the 'standard three marker' type of questions.

Unless a numerical question specifically requires evidence of working to be shown, full marks should be given for a **correct** answer to a numerical question even if the steps are not shown explicitly. The individual marks shown below are for use when marking partially correct answers.

Markers who are new to marking SQA Practical Electronics exams should study these issues closely, since the guidance illustrates common faults in candidates' answers to the 'standard three marker' type of question. Items 1-15 below illustrate how to apportion marks accordingly.

Experienced markers should also re-acquaint themselves with these examples before marking.

For some questions requiring numerical calculations, there may be alternative methods (eg alternative relationships) which would lead to a correct answer. These alternative methods of reaching the answer and how to apportion marks are also included in the specific MIs for these questions.

Sometimes, a question requires a calculation which does not fit into the 'standard three marker' type of response. Full guidance on how to apportion marks will be given in the MIs for that specific question.

**Question:**

The current in a resistor is 1.5 amperes when the potential difference across it is 7.5 volts. Calculate the resistance of the resistor. (3 marks)

Candidate answer	Mark + Comment
1. $V = IR$ $7.5 = 1.5R$ $R = 5.0 \Omega$	1 mark: formula 1 mark: substitution 1 mark: correct answer
2. $5.0 \Omega$	3 marks: correct answer
3. $5.0$	2 marks: unit missing
4. $4.0 \Omega$	0 marks: no evidence, wrong answer
5. $\_\_ \Omega$	0 marks: no working or final answer
6. $R = \frac{V}{I} = \frac{7.5}{1.5} = 4.0 \Omega$	2 marks: arithmetic error
7. $R = \frac{V}{I} = 4.0 \Omega$	1 mark: formula only
8. $R = \frac{V}{I} = \_\_ \Omega$	1 mark: formula only
9. $R = \frac{V}{I} = \frac{7.5}{1.5} = \_\_ \Omega$	2 marks: formula and substitution, no final answer
10. $R = \frac{V}{I} = \frac{7.5}{1.5} = 4.0$	2 marks: formula and substitution, wrong answer
11. $R = \frac{V}{I} = \frac{1.5}{7.5} = 5.0 \Omega$	1 mark: formula but wrong substitution
12. $R = \frac{V}{I} = \frac{75}{1.5} = 5.0 \Omega$	1 mark: formula but wrong substitution
13. $R = \frac{I}{V} = \frac{1.5}{7.5} = 5.0 \Omega$	0 marks: wrong formula
14. $V = IR$ $7.5 = 1.5 \times R$ $R = 0.2 \Omega$	2 marks: formula and substitution, arithmetic error
15. $V = IR$ $R = \frac{I}{V} = \frac{1.5}{7.5} = 0.2 \Omega$	1 mark: formula correct but wrong rearrangement of symbols

Marking instruction for each question

Question		Expected response	Max mark	Additional guidance						
1.	(a)	<p>Changes electrical energy to sound (energy) (1 mark)</p> <p>Electrolytic capacitor (1 mark)</p>  (1 mark)	3	<p>Do not accept changes <b>electricity</b> to sound</p> <p>Must state electrolytic</p>						
	(b)	<table border="1"> <thead> <tr> <th>1st band</th> <th>2nd band</th> <th>multiplier</th> </tr> </thead> <tbody> <tr> <td>yellow</td> <td>violet</td> <td>red</td> </tr> </tbody> </table>	1st band	2nd band	multiplier	yellow	violet	red	2	<p>1 mark for both colour bands</p> <p>1 mark for multiplier colour band</p>
1st band	2nd band	multiplier								
yellow	violet	red								
	(c) (i)	<p>250 <math>\Omega</math></p> <p><b>OR</b></p> <p>250R</p>	1	<p>Answer must have ohms unit or R notation</p>						
	(ii)	<p>Min = 225 <math>\Omega</math> <b>OR</b> 225R (1 mark)</p> <p>Max = 275 <math>\Omega</math> <b>OR</b> 275R (1 mark)</p>	2	<p>Accept answer consistent with 1(c)(i)</p>						
2.		<p>Cable tv, telephone cabling, secure landline communications cabling, broadband (1 mark)</p> <p>Computer cabling, internal connections inside mobile phones Computer peripheral cabling (1 mark)</p>	2	<p>Any two suitable answers.</p>						



Question			Expected response	Max mark	Additional guidance
3.	(a)	(i)	20 Ω <b>OR</b> 20 R	1	Answer must have ohms unit or R notation
		(ii)	$V = IR$ (1 mark) $6 = I \times 20$ (1 mark) $I = 0.3 \text{ A}$ (1 mark)	3	Accept answer consistent with 3(a)(i)
	(b)	(i)	$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$ (1 mark) $\frac{1}{R_T} = \frac{1}{20} + \frac{1}{5}$ (1 mark) $R_T = 4\Omega$ (1 mark)	3	$R_T = \frac{R_2 R_3}{R_2 + R_3}$ Is an acceptable alternative method If wrong equation used, eg $R_T = \frac{1}{R_2} + \frac{1}{R_3}$ then (0) marks. Accept imprecise working towards a final answer. $\frac{1}{R_T} = 4\Omega$ ↑ Accept Accept = 4 R Accept any subscript on component resistors
		(ii)	6V (1 mark)	1	Answer must have unit

Question		Expected response	Max mark	Additional guidance															
	(iii)	$P = \frac{V^2}{R} \quad (1 \text{ mark})$ $P = \frac{6^2}{5} \quad (1 \text{ mark})$ $P = 7.2 \text{ W} \quad (1 \text{ mark})$	3	Accept answer consistent with 3(b)(ii)  Both equations            1 mark Both substitutions       1 mark Answer and unit         1 mark  $V = IR$  $6 = I \times 5$ $I = 1.2(A)$ $P = IV$ $P = 1.2 \times 6$ $P = 7.2W$  <b>OR</b>  $P = I^2R$ $R = 1.2^2 \times 5$ $P = 7.2W$															
4.	(a)	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	A	B	Output	0	0	1	0	1	1	1	0	1	1	1	0	1	
A	B	Output																	
0	0	1																	
0	1	1																	
1	0	1																	
1	1	0																	

Question		Expected response	Max mark	Additional guidance																																																															
	(b)	0	1																																																																
	(c)	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> <th>D</th> <th>E</th> <th>Y</th> <th>Z</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> <td>0</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> <td>0</td> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>0</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>0</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td>0</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> <td>1</td> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> <td>0</td> <td>0</td> </tr> </tbody> </table>	A	B	C	D	E	Y	Z	0	0	0	0	0	1	0	0	0	1	0	1	0	1	0	1	0	0	0	1	0	0	1	1	0	1	0	1	1	0	0	0	1	0	1	1	0	1	0	1	0	1	1	1	0	1	1	0	0	1	1	1	1	1	0	0	4	<p>1 mark per column</p> <p>Apply follow through between columns</p>
A	B	C	D	E	Y	Z																																																													
0	0	0	0	0	1	0																																																													
0	0	1	0	1	0	1																																																													
0	1	0	0	0	1	0																																																													
0	1	1	0	1	0	1																																																													
1	0	0	0	1	0	1																																																													
1	0	1	0	1	0	1																																																													
1	1	0	1	1	0	0																																																													
1	1	1	1	1	0	0																																																													

Question		Expected response	Max mark	Additional guidance																																
5.	(a)	Connect red wire of probe to $V_{\text{supply}}$ and black wire to 0 V (1 mark)	1	Do not accept: connect the probe to the supply rails (on its own)																																
	(b)	Place the probe tip onto circuit at selected point (1 mark)  Green LED lights (1 mark)	2																																	
6.		Supply voltage too high (1 mark)  LED wrong way round (1 mark)  Protective resistor for LED has too low a resistance (1 mark)  Transistor should be a npn/mosfet (1 mark)  <b>OR</b>  LDR and variable resistor should be changed over position in circuit (1 mark)	4	Errors can be listed in any order																																
7.		<table border="1"> <tbody> <tr> <td>Measuring supply voltage</td> <td>Instrument multimeter voltage setting</td> </tr> <tr> <td>Output logic level from gate</td> <td>Logic probe</td> </tr> <tr> <td>Voltage across LED</td> <td>Multimeter voltage setting</td> </tr> </tbody> </table>	Measuring supply voltage	Instrument multimeter voltage setting	Output logic level from gate	Logic probe	Voltage across LED	Multimeter voltage setting	2	1 mark for each row  Accept logic level  Accept voltmeter Do not accept multi-meter on its own																										
Measuring supply voltage	Instrument multimeter voltage setting																																			
Output logic level from gate	Logic probe																																			
Voltage across LED	Multimeter voltage setting																																			
8.		<table border="1"> <thead> <tr> <th>Supplier</th> <th>Component</th> <th>Product code</th> <th>Cost (p)</th> </tr> </thead> <tbody> <tr> <td>JIMSON</td> <td>NE555</td> <td>TC124</td> <td>20</td> </tr> <tr> <td>SWIFT</td> <td>8 way DIL socket</td> <td>SK-0080</td> <td>10</td> </tr> <tr> <td>SWIFT</td> <td>LED 5mm std</td> <td>SC-0155</td> <td>4</td> </tr> <tr> <td>JIMSON</td> <td>100<math>\mu</math>F electrolytic capacitor</td> <td>EC 800</td> <td>10</td> </tr> <tr> <td>SWIFT</td> <td>100nF capacitor</td> <td>CP-2030</td> <td>35</td> </tr> <tr> <td>JIMSON</td> <td>270R</td> <td>FR 922</td> <td>0.25</td> </tr> <tr> <td>JIMSON</td> <td>4K7</td> <td>FR 923</td> <td>0.25</td> </tr> </tbody> </table>	Supplier	Component	Product code	Cost (p)	JIMSON	NE555	TC124	20	SWIFT	8 way DIL socket	SK-0080	10	SWIFT	LED 5mm std	SC-0155	4	JIMSON	100 $\mu$ F electrolytic capacitor	EC 800	10	SWIFT	100nF capacitor	CP-2030	35	JIMSON	270R	FR 922	0.25	JIMSON	4K7	FR 923	0.25	5	1 mark for each row
Supplier	Component	Product code	Cost (p)																																	
JIMSON	NE555	TC124	20																																	
SWIFT	8 way DIL socket	SK-0080	10																																	
SWIFT	LED 5mm std	SC-0155	4																																	
JIMSON	100 $\mu$ F electrolytic capacitor	EC 800	10																																	
SWIFT	100nF capacitor	CP-2030	35																																	
JIMSON	270R	FR 922	0.25																																	
JIMSON	4K7	FR 923	0.25																																	

Question		Expected response	Max mark	Additional guidance
9.	(a)	500 $\Omega$ <b>OR</b> 500R	1	
	(b)	$V_2 = \frac{R_2}{R_1 + R_2} \times V_s \quad (1 \text{ mark})$ $V_2 = \frac{500}{(3250 + 500)} \times 6 \quad (1 \text{ mark})$ $V_2 = 0.8V \quad (1 \text{ mark})$	3	Accept answer consistent with 9(a)  $V = IR$ $6 = I \times 3750$ $I = 0.0016$ $I = 1.6 \times 10^{-3} (A)$ $V = IR$ $V = 1.6 \times 10^{-3} \times 500$ $V = 0.8V$  1 mark for Ohm's Law anywhere. 1 mark for both substitutions. 1 mark for final answer including unit.  Or by voltage ratio method.  If correct answer given with no working award 3 marks.
	(c)	As light level reduces LDR resistance increases <b>(1 mark)</b>  As LDR resistance increases the voltage across LDR increases. <b>(1 mark)</b>  When voltage across the LDR reaches 0.8V transistor switches on <b>(1 mark)</b>	3	

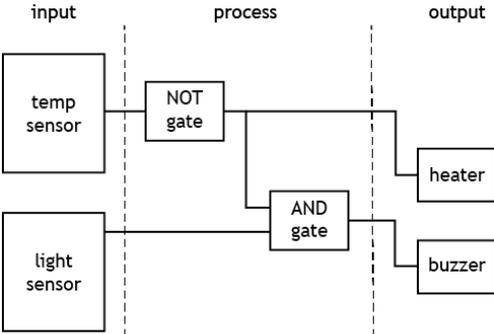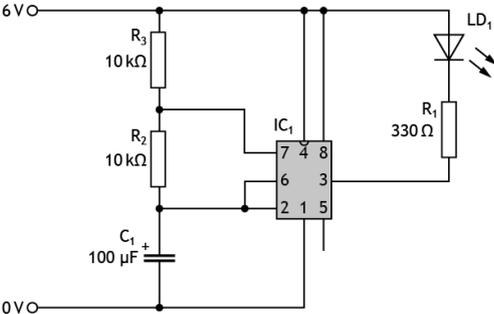Question	Expected response	Max mark	Additional guidance
10.	<p>1 mark for selecting both input devices</p> <p>1 mark for selecting correct gates</p> <p>1 mark for selecting both output devices</p> <p>1 mark for correctly linking the inputs and gates</p> <p>1 mark for correctly linking outputs to the gates</p> <p>1 mark for correctly identifying the three sections of the system</p>	6	 <p>All selected elements must be shown as part of a system/block diagram. (arrows are NOT required on the connections).</p>
11.	<p>Both power rails labelled with nodes (1 mark)</p> <p>Power rails to IC (4,8 to +6V and 1 to 0V) (1 mark)</p> <p>The “output” +6V to pin 3 via R<sub>1</sub> and correctly orientated LED (1 mark)</p> <p>R<sub>2</sub>,R<sub>3</sub> and C<sub>1</sub> in series between power rails with C<sub>1</sub> correctly orientated (1 mark)</p> <p>For 6,7 and 2 connected, 5 not connected (1 mark)</p> <p>Component labelling (1 mark)</p>	6	 <p>Accept a mixture of identifiers and values</p> <p>Accept R notation</p>

[END OF MARKING INSTRUCTIONS]