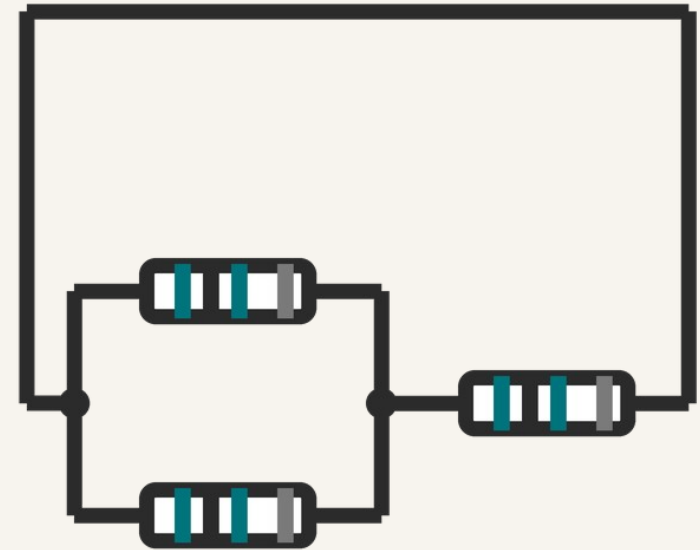


Combining Resistors 2

Branches of different values, and circuits that mix series with parallel.

N5 Physics and Electronics (S3)



Daily Review

Booklet p.11-12 — Combining Resistors 1

- 1 Write the relationship for resistors in series.
- 2 Three $100\ \Omega$ resistors are in series. Find R_T .
- 3 Four $200\ \Omega$ resistors are in parallel. Find R_T .
- 4 Is a parallel total bigger or smaller than one branch?
- 5 Where do the two probes go to measure a total resistance?

PART 1

Different Values

The easy rule only worked because every branch was the same.

By the end of this part...

- 1 I can predict the total resistance of parallel branches of different values
- 2 I can measure that total resistance with an ohmmeter
- 3 I can solve problems involving total resistance in a parallel circuit

Why the easy rule fails

Booklet p.13

- Equal branches take equal shares of the current.
- Unequal branches do not — the smaller resistance takes more.
- So every branch has to be counted separately, one at a time.

The relationship

Booklet p.13 – branches of different values

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

R_T

the total resistance of the combination, in ohms (Ω)

R_1, R_2

the separate branches, in ohms (Ω)

Worked example 1

Two branches of different values

Find the total resistance of a 470 Ω and a 220 Ω resistor in parallel.

$$R_1 = 470 \Omega$$

$$R_2 = 220 \Omega$$

$$R_T = ?$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{1}{470} + \frac{1}{220}$$

$$\frac{1}{R_T} = 0.006673$$

$$\underline{R_T = 149.9 \Omega}$$

Watch out

THE MISTAKE

- Stopping at $1/R_T = 0.006673$
- Adding $470 + 220$ for a parallel pair
- An answer bigger than one of the branches

THE CORRECT ANSWER

- Invert it — $R_T = 149.9 \Omega$
- Add the reciprocals, then invert
- Always less than the smallest branch — check it

Task 1 – name the three rules

Booklet p.13

Three relationships are printed with a blank
beside each.

Write in the word that finishes the sentence.

Booklet p.13, Task 1

Task 1 – Answers

ANSWERS

Booklet p.13 – the three relationships

	The blank	When you use it
1	series	resistors one after another
2	parallel	branches, all the same value
3	parallel	branches, different values

Show me — different values in parallel

SHOW ME BOARDS

- 1 A $10\ \Omega$ and a $15\ \Omega$ resistor in parallel. Find R_T .
- 2 A $20\ \Omega$ and a $30\ \Omega$ resistor in parallel. Find R_T .
- 3 A $6\ \Omega$ and a $3\ \Omega$ resistor in parallel. Find R_T .
- 4 A $100\ \Omega$ and a $400\ \Omega$ resistor in parallel. Find R_T .
- 5 A $2\ \Omega$, a $3\ \Omega$ and a $6\ \Omega$ resistor in parallel. Find R_T .

Show me – different values in parallel

SHOW ME BOARDS

EXTRA PRACTICE

- 1 A $12\ \Omega$ and a $4\ \Omega$ resistor in parallel. Find R_T .
- 2 A $40\ \Omega$ and a $60\ \Omega$ resistor in parallel. Find R_T .
- 3 A $200\ \Omega$ and a $50\ \Omega$ resistor in parallel. Find R_T .
- 4 A $5\ \Omega$ and a $20\ \Omega$ resistor in parallel. Find R_T .
- 5 A $30\ \Omega$, a $20\ \Omega$ and a $12\ \Omega$ resistor in parallel. Find R_T .

Daily Review

Booklet p.13 – different values in parallel

- 1 Write the relationship for parallel branches of different values.
- 2 Two $10\ \Omega$ resistors in parallel. Find R_T .
- 3 A $30\ \Omega$ and a $15\ \Omega$ resistor in parallel. Find R_T .
- 4 What must you do to $1/R_T$ at the end of the calculation?
- 5 Can the total be bigger than the smallest branch?

PART 2

Combination Circuits

Series and parallel in the same circuit. Take it one block at a time.


By the end of this part...

- 1 I can find the parallel block in a combination circuit
- 2 I can replace that block with a single resistance
- 3 I can solve problems involving total resistance in a combination circuit

The method


Booklet p.13

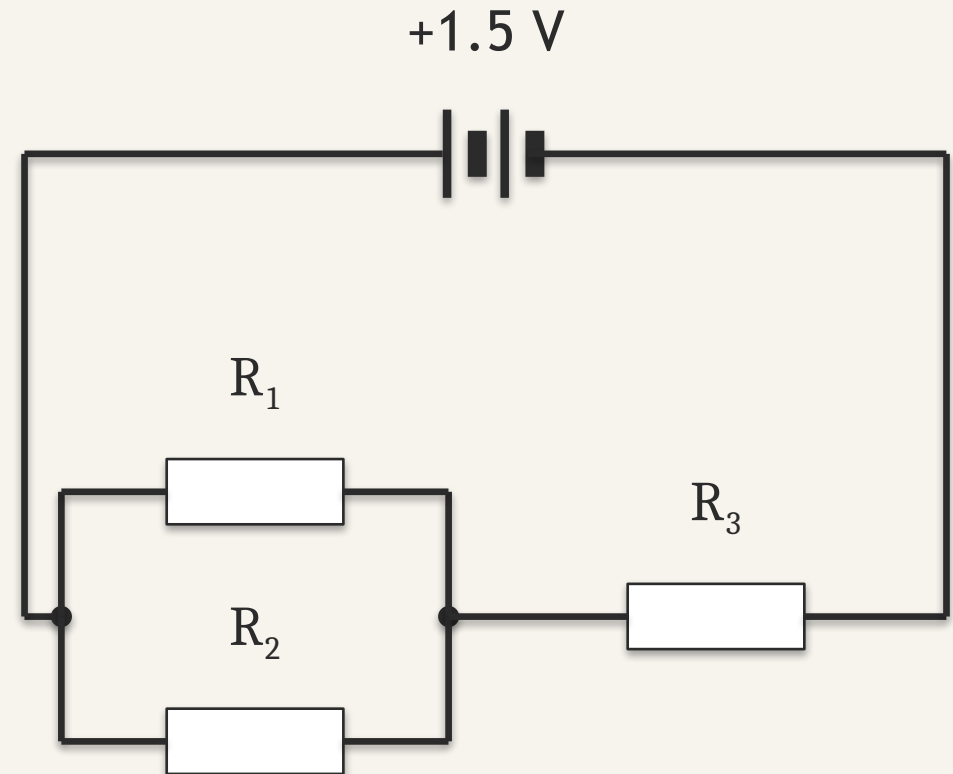- Find the parallel block and work it out on its own.
- Replace the whole block with one resistance.
- Add that to whatever is in series with it.



The booklet's worked example

Booklet p.13 – the circuit

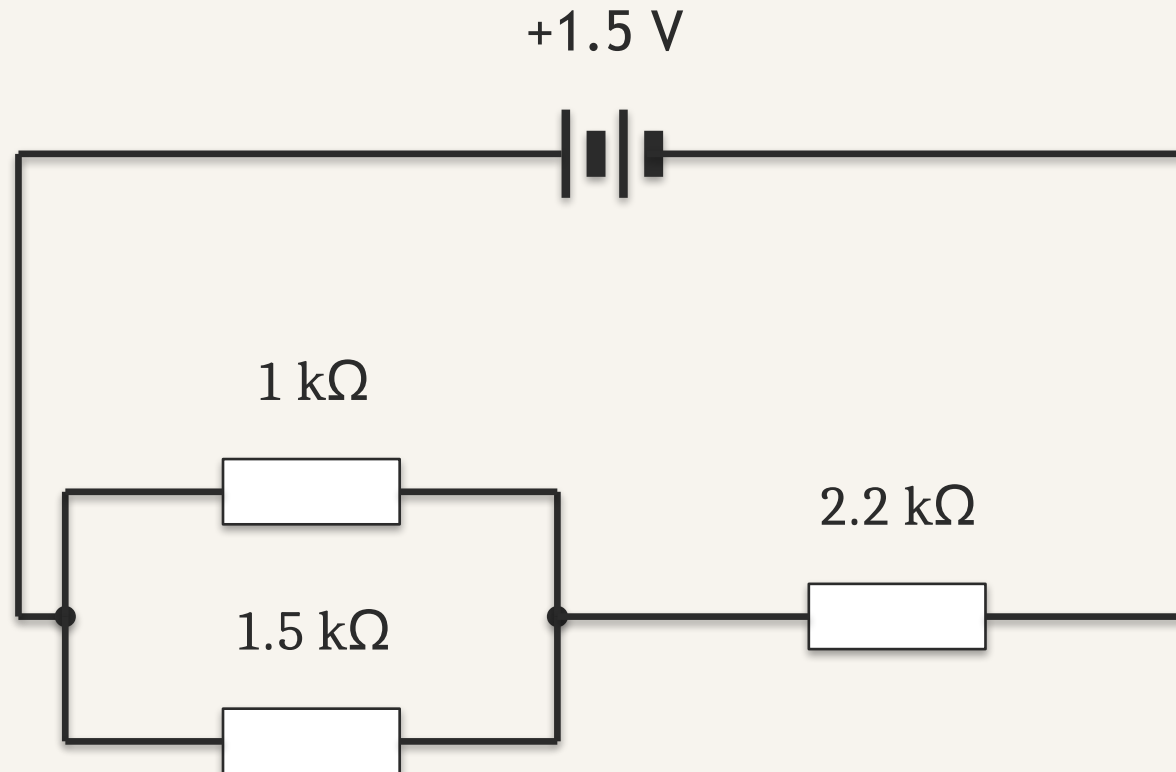

Step 1 – the parallel block

Booklet p.13

Calculate the resistance of the 1 kΩ and 1.5 kΩ parallel block.

$$R_1 = 1000 \, \Omega$$

$$R_2 = 1500 \, \Omega$$

$$R_p = ?$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_p} = \frac{1}{1000} + \frac{1}{1500}$$

$$\frac{1}{R_p} = 0.001667$$

$$\underline{R_p = 600 \, \Omega}$$

Step 2 – add the series resistor

Booklet p.14

The $600\ \Omega$ block is **in series** with the $2.2\ \text{k}\Omega$ resistor.
Calculate the total resistance of the whole circuit.

$$R_P = 600\ \Omega$$

$$R_3 = 2200\ \Omega$$

$$R_T = ?$$

$$R_T = R_P + R_3$$

$$R_T = 600 + 2200$$

$$\underline{R_T = 2800\ \Omega = 2.8\ \text{k}\Omega}$$

Task 2 – four circuits

Booklet p.14

Four combination circuits.
Work out the parallel block first, then finish.

Booklet p.14, Task 2

Task 2 – Answers, circuits 1 and 2

ANSWERS

Booklet p.14

	Step 1 – the parallel block	Step 2 – the series part
1	100 Ω with 200 Ω : 66.7 Ω	66.7 + 750 = 817 Ω
2	3.5 k Ω with 1.5 k Ω : 1050 Ω	1050 + 10 000 = 11 050 Ω

That is 817 Ω and 11.05 k Ω .

Task 2 – Answers, circuits 3 and 4

ANSWERS

Booklet p.14

	Step 1 – the series pair	Step 2 – the parallel block
3	$1.0\text{ k}\Omega + 2.2\text{ k}\Omega = 3.2\text{ k}\Omega$	$3.2\text{ k}\Omega$ with $1.5\text{ k}\Omega$: $1.02\text{ k}\Omega$
4	$7.5\text{ k}\Omega + 2.2\text{ k}\Omega = 9.7\text{ k}\Omega$	$9.7\text{ k}\Omega$ with $750\text{ }\Omega$: $696\text{ }\Omega$

Here the series pair comes first, then the parallel block.

Task 3 – more practice

Booklet p.15

Work the Yellow Book resistance questions.
Then sit the check test and mark it yourself.

Booklet p.15, Task 3
Yellow Books p.42-44
N5 Electricity CT 4 – Practical Circuits

Checkpoint

- 1 Write the relationship for parallel branches of different values.
- 2 A $12\ \Omega$ and a $6\ \Omega$ resistor are in parallel. Find R_T .
- 3 In a combination circuit, which part do you work out first, and why?

LOOKING AHEAD

Review and Test Prep

Everything in Booklet 1, and the practice test.

Plenary

- 1 Write the relationship for different values in parallel.
- 2 A $20\ \Omega$ and a $5\ \Omega$ resistor in parallel. Find R_T .
- 3 What is the last step of a parallel calculation?
- 4 Two $40\ \Omega$ resistors in parallel, then $30\ \Omega$ in series. Find R_T .
- 5 Why is a parallel total always less than its smallest branch?

Plenary

EXTRA PRACTICE

- 1 A $3\ \Omega$ and a $6\ \Omega$ resistor in parallel. Find R_T .
- 2 Two $100\ \Omega$ resistors in parallel, then $50\ \Omega$ in series. Find R_T .
- 3 Which block do you work out first in a combination circuit?
- 4 Two $24\ \Omega$ resistors in parallel. Find R_T .
- 5 Give $2800\ \Omega$ in kilohms.

Extension

- 1 A $6\ \Omega$, a $12\ \Omega$ and a $4\ \Omega$ resistor, all in parallel. Find R_T .
- 2 A $10\ \Omega$ resistor in series with two $20\ \Omega$ resistors that are in parallel with each other. Find R_T .
- 3 You have three $30\ \Omega$ resistors. List every total you can make using all three of them.

Extension

EXTRA PRACTICE

- 1 A $5\ \Omega$ and a $20\ \Omega$ resistor in parallel, then $6\ \Omega$ in series. Find R_T .
- 2 Two resistors in parallel give $8\ \Omega$. One of them is $24\ \Omega$. Find the other.
- 3 Explain why putting anything in parallel with a $10\ \Omega$ resistor can never give more than $10\ \Omega$.

Exam practice

Past-paper questions on this topic

- 1 2024 Paper 1 — questions 11, 12 and 13
- 2 2022 Paper 1 — questions 12, 13 and 14

© Qualifications Scotland (SQA) — questions are cited, not reproduced.